





ALEX,  
TRANSISTOR TRACY AND CAPACITOR CARL  
PRESENT:


EVERYTHING YOU WANTED  
TO KNOW ABOUT

MOTOR CONTROL




BUT WERE AFRAID TO ASK



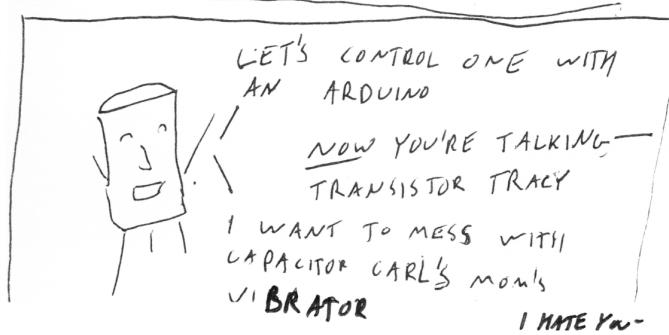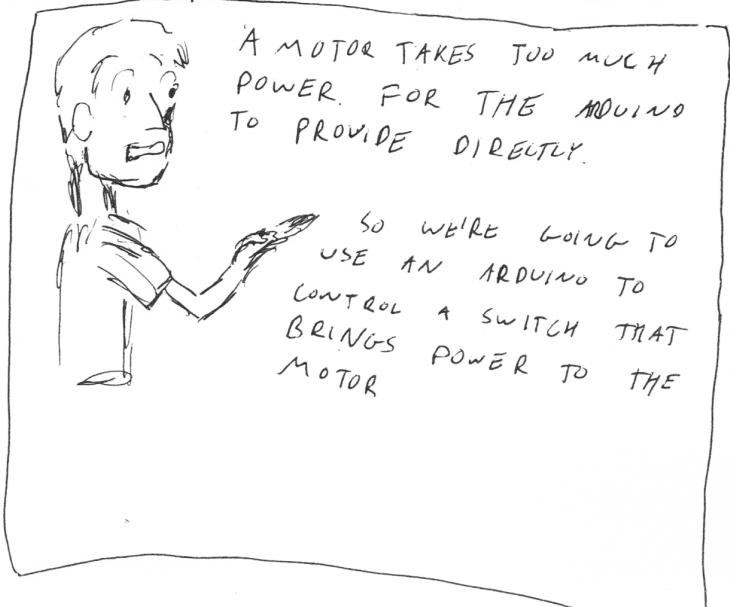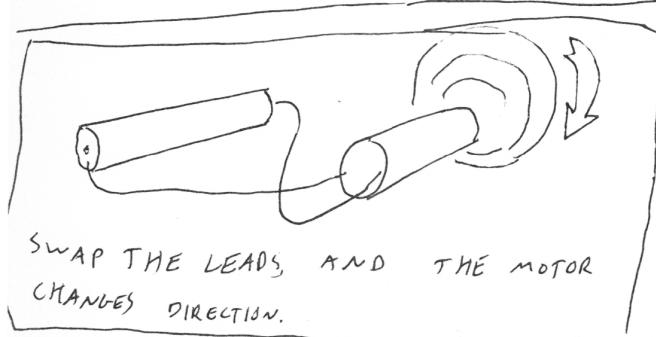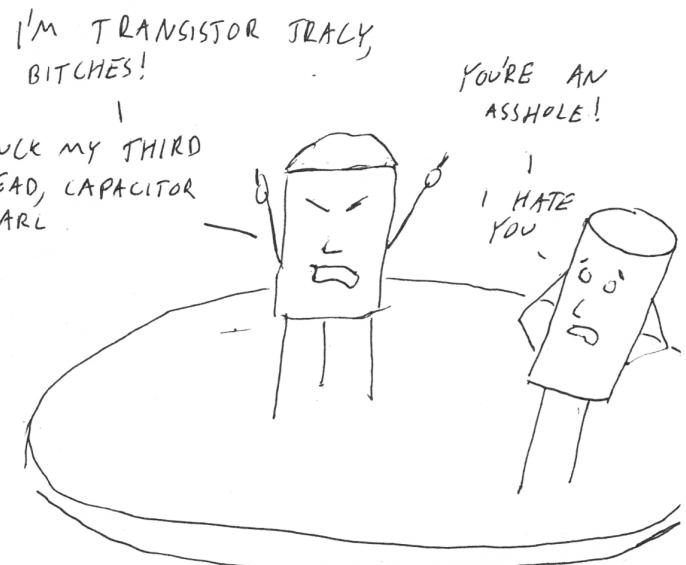


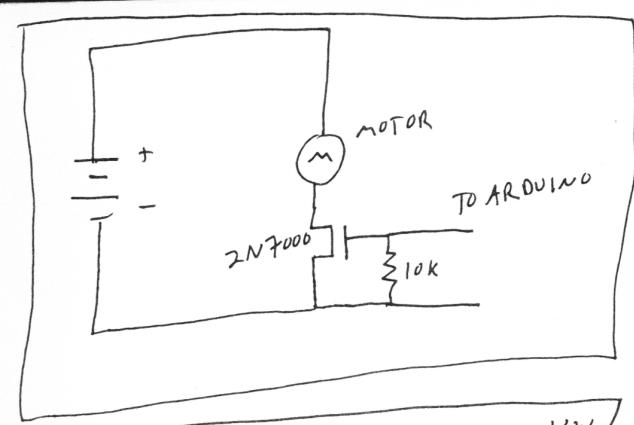

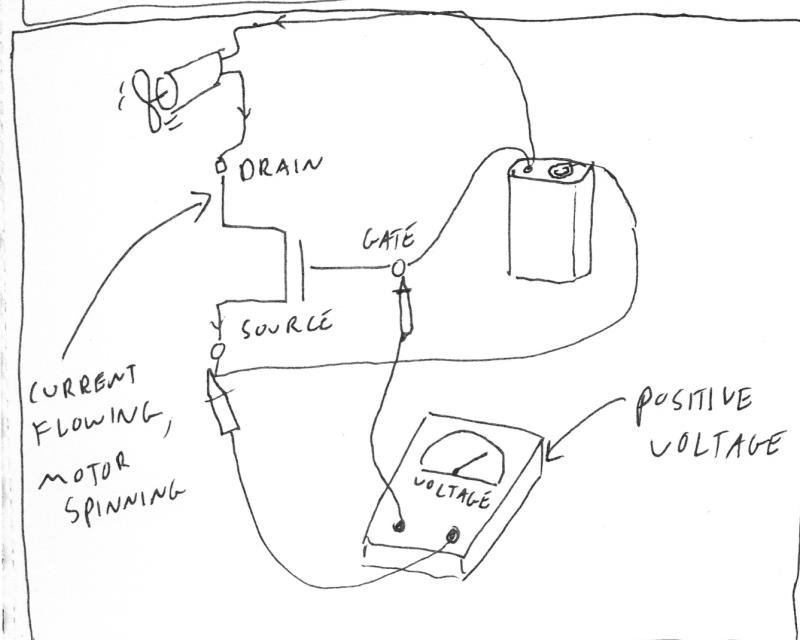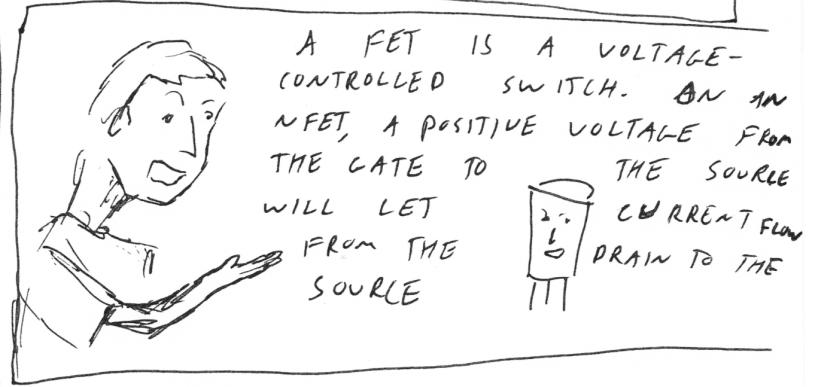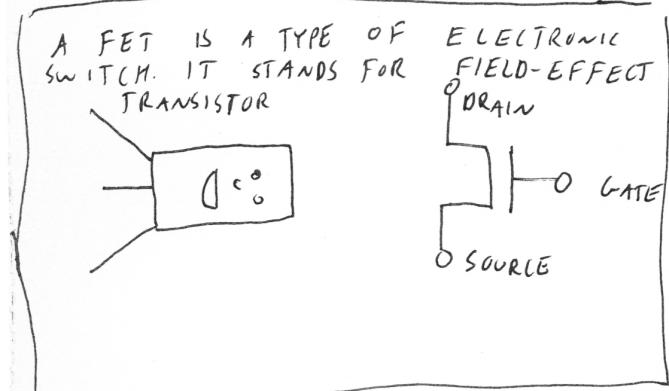SO, HERE'S THE BASIC CIRCUIT:  
WE'RE USING A FET TO SWITCH  
POWER TO THE MOTOR. THE ARDUINO  
CONTROLS THE FET'S GATE



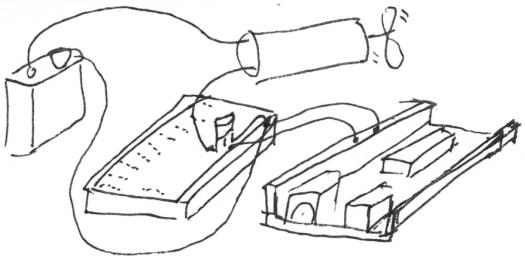AND WE CAN USE A SMALL SIGNAL, LIKE ONE FROM THE ARDUINO'S OUTPUT PIN, TO SWITCH A FET AND CONTROL A LARGE LOAD, LIKE A MOTOR



SO HERE, WE HAVE AN ARDUINO CONTROLLING A MOTOR. IF THE ARDUINO'S OUTPUT PIN GOES HIGH (+5V), THE FET ALLOWS CURRENT TO FLOW AND THE MOTOR SPINS. IF IT GOES LOW, THE MOTOR TURNS OFF.

BUT WHAT IF WE WANT THE MOTOR TO SPIN AT DIFFERENT SPEEDS? WE COULD FIND BIGGER OR SMALLER BATTERIES AND CHANGE BATTERIES FOR EACH SPEED, BUT THAT'S NOT VERY ELEGANT... UNLIKE CARL'S MOM SHUT UP! DUDE, YOUR MOM'S A FOX



SO HERE, CARL'S CONNECTING THE VOLTAGE TO THE GATE FOR A SECOND, AND THEN DISCONNECTING IT FOR A SECOND.



THE MOTOR'S MOTION IS VERY JERKY, BUT ITS AVERAGE SPEED IS  $\frac{1}{2}$  ITS MAX SPEED, BECAUSE WE'RE ONLY GIVING IT POWER HALF THE TIME

AND IF I CONNECT AND DISCONNECT THE WIRES FASTER THAN THE MOTOR CAN PHYSICALLY RESPOND, THAT JERKINESS GOES AWAY, AND I CAN SMOOTHLY CHANGE THE MOTOR'S SPEED BY CHANGING THE PROPORTION OF TIME IT'S POWERED



THIS IS CALLED PULSE-WIDTH MODULATION, OR PWM.

THE ARDUINO HAS A BUILT-IN WAY OF GENERATING THIS KIND OF SIGNAL. IN THE ARDUINO LANGUAGE, YOU CAN USE THE COMMAND `analogWrite(pin, value)`

"PIN" IS THE PIN NUMBER YOU'RE USING TO CONTROL THE FET, AND "VALUE" IS A NUMBER REPRESENTING THE MOTOR'S SPEED, WITH 0 BEING COMPLETELY STOPPED AND 1023 BEING FULL SPEED

SO NOW WE CAN CONTROL A DC MOTOR'S SPEED



BUT I WANT THE MOTOR TO SPIN BACKWARDS! HOW CAN I DO THAT?

I'M SO VERY GLAD YOU ASKED...




TO MAKE A MOTOR SPIN BACKWARDS, I JUST SWAP THE WIRES TO THE POWER SUPPLY. EASY-PEASY




LIKE YER  
MOM! OH!

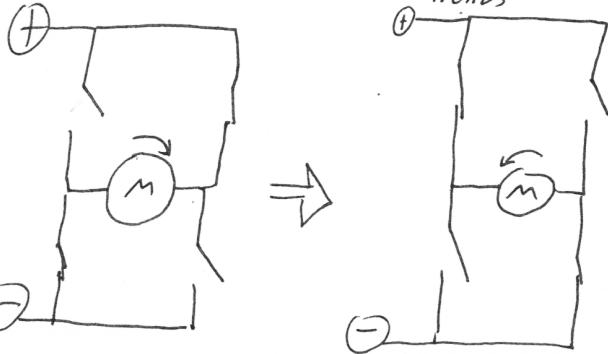INSTEAD OF SWAPPING THE WIRES, I CAN CHANGE THE VOLTAGE APPLIED TO THE MOTOR ELECTRONICALLY, WITH FOUR SWITCHES



US ENGINEERS CALL THIS SET OF SWITCHES AN "H-BRIDGE"

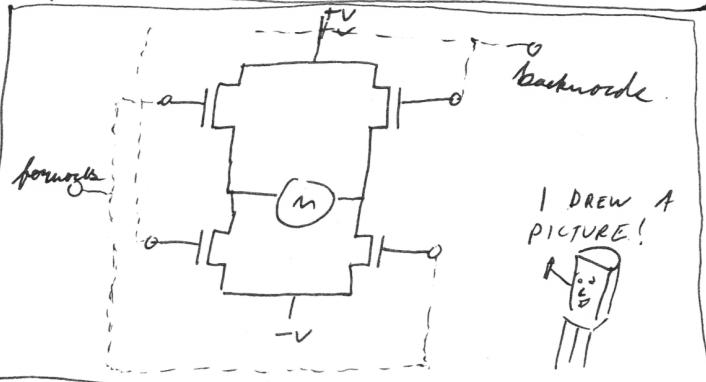AND IF YOU USE TRANSISTORS INSTEAD OF SWITCHES, YOU CAN CONTROL THE DIRECTION OF A MOTOR ELECTRONICALLY




I'M TOO LAZY TO WIRE UP ALL THOSE TRANSISTORS, SO I USUALLY USE AN H-BRIDGE CHIP, THE L293




IT'S A LITTLE MORE EXPENSIVE, BUT IT'S VERY CONVENIENT

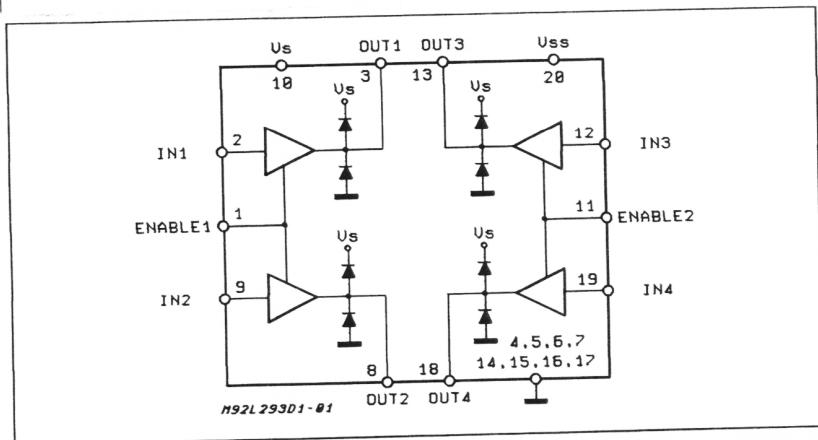IT ALSO HAS A HANDY FEATURE CALLED CRANKY MOTORS THAT KEEP OUR ELECTRONICS FROM BLOWING UP



HERE'S HOW TO CONNECT

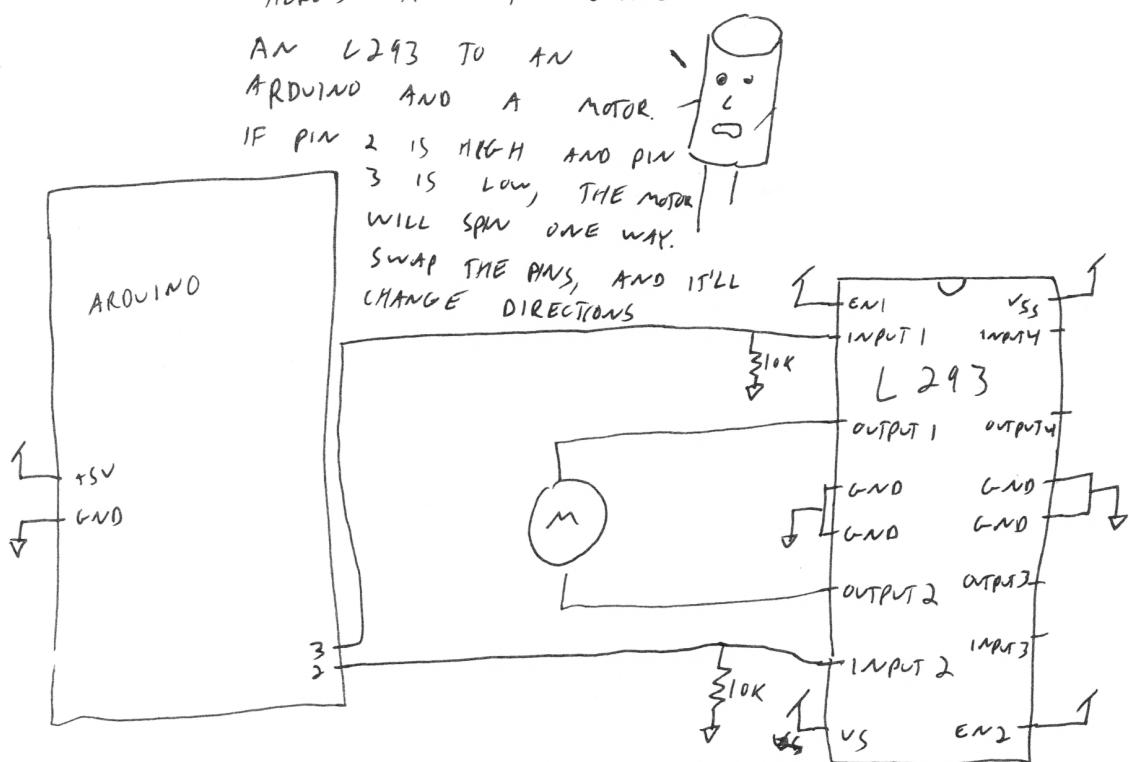AN L293 TO AN  
ARDUINO AND A MOTOR.  
IF PIN 2 IS HIGH AND PIN  
3 IS LOW, THE MOTOR  
WILL SPIN ONE WAY.  
SWAP THE PINS, AND IT'LL  
CHANGE DIRECTIONS



HEY ASS-BUTT!

DON'T FORGET TO MENTION THAT YOU  
CAN PWM THE ARDUINO PINS TO  
CONTROL THE MOTOR SPEED

THE SLACKERS AMONG YOU CAN  
COPY MY FUCKING OPEN-SOURCE  
CODE TO MAKE THE SHEEZY HAPPEN  
ON YOUR ARDUINOS:

THE 10K RESISTORS ARE  
CALLED "PULL-DOWN" RESISTORS.  
WITHOUT THEM, THE  
L293'S FEELS  
DON'T ALWAYS  
TURN OFF, EVEN  
IF THE ARDUINO'S  
PINS ARE LOW

~~digital~~ analogWrite(3, 900);  
digitalWrite(2, LOW); // SPIN THE MOTOR ONE WAY AT  
~90% SPEED

digitalWrite(3, LOW)  
analogWrite(2, 200) // SPIN THE MOTOR THE OTHER WAY  
AT ~20% SPEED

\* THIS CODE WAS WRITTEN BY TRACY  
OTHER ANYBODY USING IT FOR ANYTHING  
DICK AND HAS A SMELLY VENEREAL DISEASE \*

HEY GUYS!

LOOK WHAT I FOUND LYING AROUND!



NICE STEPPER, MAN.

SHE LOOKS BIPOLAR TO ME

I DON'T THINK IT'S VERY NICE TO TALK ABOUT SOMEONE'S ISSUES LIKE THAT


NO, NO.

THAT'S THE TYPE OF MOTOR

IT'S ALL ABOUT HER COILS

& SNICKER

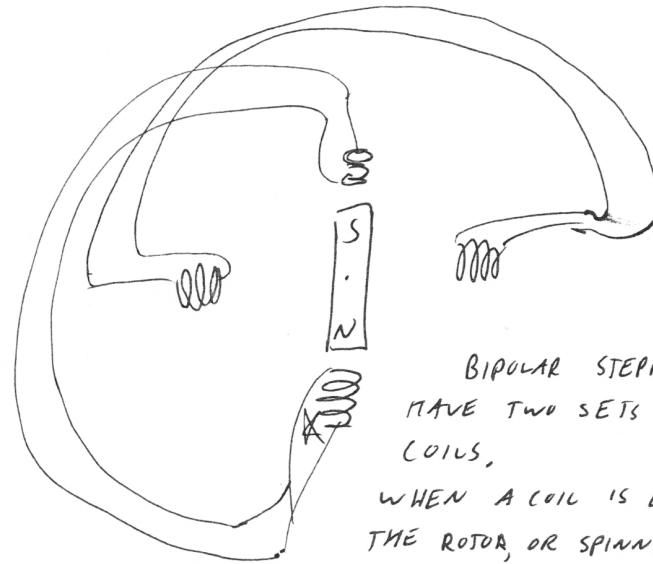
BIPOLAR MOTORS HAVE FOUR WIRES - THAT'S HOW YOU CAN TELL



BIPOLAR STEPPERS

HAVE TWO SETS OF COILS,

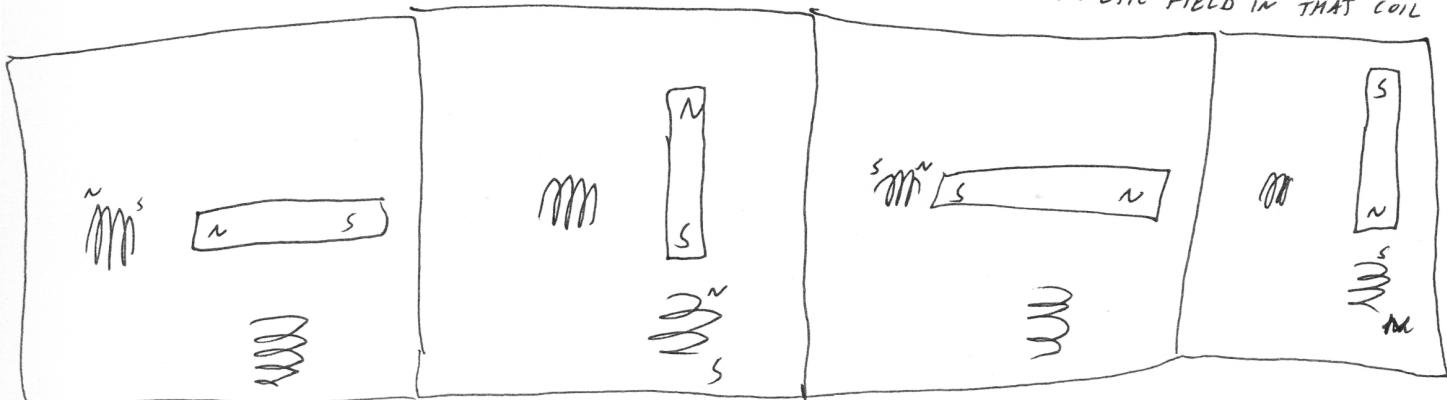WHEN A COIL IS ENERGIZED, THE ROTOR, OR SPINNY-BIT, ALIGNS WITH THE MAGNETIC FIELD IN THAT COIL



BY "STEPPING" THROUGH THE COILS, WE CAN MAKE THE ROTOR SPIN COMPLETELY AROUND



HOORAY!




WITH BIPOLAR STEPPERS, WE  
HAVE TO CHANGE THE DIRECTION  
OF CURRENT THROUGH THE COILS.



UNIPOLARS ARE A LITTLE SIMPLER.  
THEY HAVE FOUR SETS OF COILS,  
AND WE ONLY HAVE TO TURN  
EACH ONE ON IN ONE DIRECTION



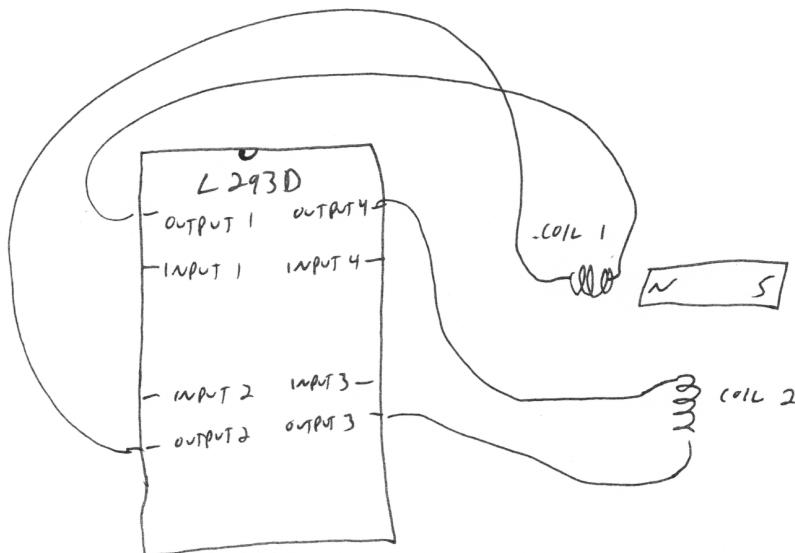FORTUNATELY, WE JUST  
LEARNED HOW TO  
MAKE CURRENT GO  
IN BOTH DIRECTIONS  
THROUGH A COIL  
REMEMBER THE H-BRIDGE?  
WE CAN USE IT TO  
CONTROL A STEPPER, TO



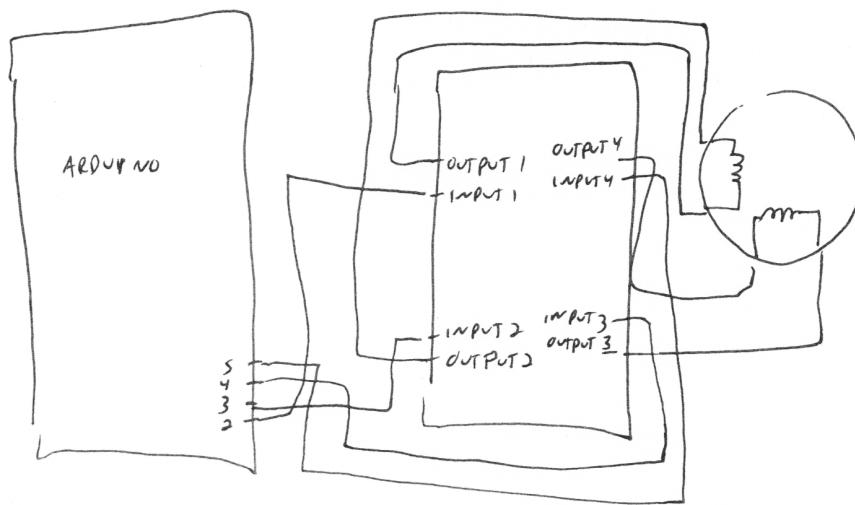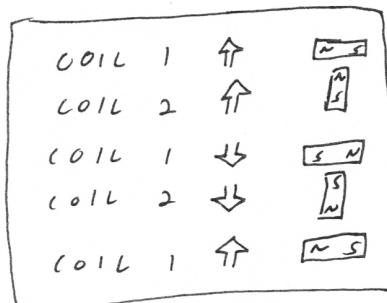NOW, WE JUST HAVE TO TURN  
THE COILS ON IN A CERTAIN  
ORDER, AND WE CAN MAKE  
THIS PUPPY SPIN



```
digitalWrite(2, HIGH)
delay(10)
digitalWrite(2, LOW)
digitalWrite(4, HIGH)
delay(10)
digitalWrite(4, LOW)
digitalWrite(3, HIGH)
delay(10)
digitalWrite(3, LOW)
digitalWrite(5, HIGH)
delay(10)
digitalWrite(5, LOW)
```